
Performance Evaluation of an Energy Storage System for Household Applications

Dr. Christian Klumpner

Electrical Systems and Optics Division
Faculty of Engineering, University of Nottingham


klumpner@ieee.org

Future House



www.ferroamp.com/energyhub/benefits-for-consumers/

 Project Aim: Develop an Energy Storage System based on the Supercapattery Device for household application : 1-2kWh / 2kW rated power



16 cell supercapattery stack
(120F/20V)


Chemical Engineering Track (team led by Prof. G.Z.Chen):

- Develop novel materials with high specific capacitance (F/g)
- Develop full working cells (test materials)
- Develop full working stacks

Electrical Engineering Track (Dr.Kulsangcharoen&Klumpner):

- Characterisation of Supercapattery stacks
- Cell voltage monitoring and estimation of individual cell performance
- Development of voltage equaliser
- Development of a Power Converter System
- Investigating the performance of converter using novel materials/advanced topologies

Proposed Converter System

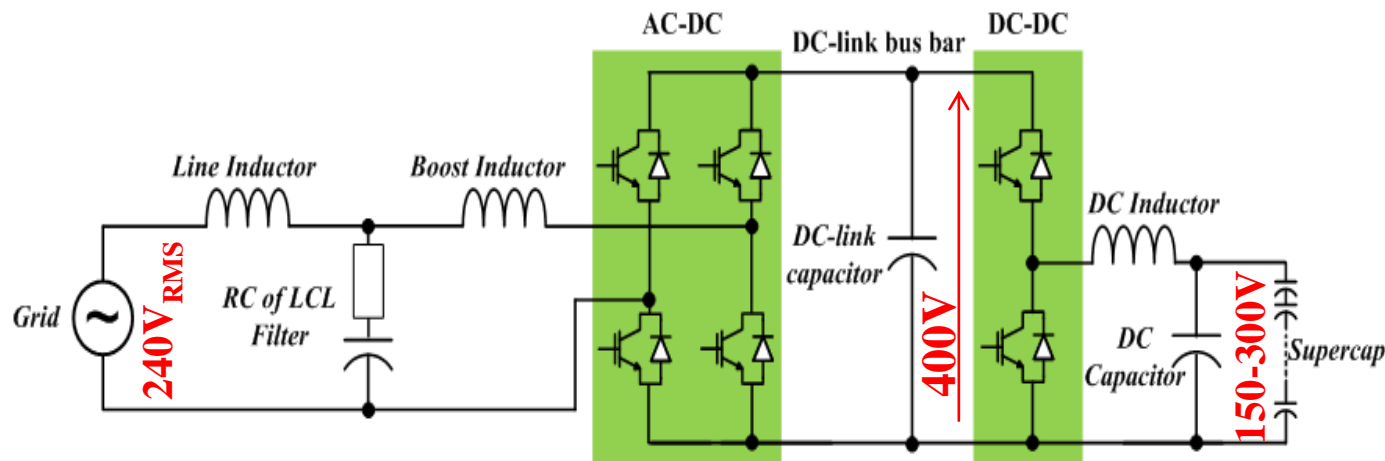


- **Employ two-stage topology consisting of:**
 - a half-bridge inverter topology for the DC variable (SC) to DC fixed voltage
 - a conventional H-bridge inverter topology for the DC/AC conversion
- The supercapacitor (SC) is operated between 150V to 300V (ratio 1:2) in order to utilise 75% of its maximum stored energy
- Fixed DC-link voltage allows for reduced switching losses and reduces size of the inductors (AC side and SC side)
- **Design Aims: Maximum conversion efficiency at a reasonable cost**
 - ⇒ use Trench/Fieldstop IGBT3 (Infineon) and metglas magnetic core material

Determine Breakdown of Power Losses



 - Design of passive components based on standard switching ripple attenuation
- Selection of devices is based on reasonable current loading 30A IGBT, $j_{co} > 2.5 \text{ A/mm}^2$
- Simulation waveforms (time domain and FFT) used in conjunction with detailed loss models of semiconductors and inductors (ESR vs frequency)
- Breakdown of power losses performed at 0.5kW/1.0kW/1.5kW/2kW and 5-10kHz



Example of Power Loss breakdown at rated power (2kW) and fsw= 5-10kHz

Optimum Switching Frequency

The total system power loss is

$$P_{TLoss} = P_{Semi} + P_{LossLDC} + P_{LossLAC} + P_{LossLBoost} + P_{LossRLCL} + P_{LossDCLink}$$

Where it is assumed current ripple is inverse proportional with switching frequency and ESR is constant or varies with frequency (curve fitting function)

$$P_{Semi} = P_{Cond} + \left\{ P_{Sw_10kHz} \cdot 10^4 / f_{sw} \right\}$$

$$P_{LossLDC} = P_{LossLDC_LF} + ESR_{LDC}(f_{sw}) \left\{ I_{LDC_10kHz} \cdot 10^4 / f_{sw} \right\}^2$$


$$P_{LossLAC} = P_{LossLAC_LF} + ESR_{LAC}(f_{sw}) \left\{ I_{LAC_20kHz} \cdot 10^4 / f_{sw} \right\}^2$$

$$P_{LossLBoost} = P_{LossLBoost_LF} + ESR_{LBoost}(f_{sw}) \left\{ I_{LBoost_20kHz} \cdot 10^4 / f_{sw} \right\}^2$$

$$P_{LossRLCL} = P_{LossRLCL_LF} + (R_{LCL}) \left\{ I_{LBoost_20kHz} \cdot 10^4 / f_{sw} \right\}^2$$

LF

HF

 


- Perform a derivative on the P_{TLoss} against f_{sw} and set it to 0.
- Solve this new equation, the optimum f_{sw} can be determined (f_{swBest} where P_{TLoss} is at its minimum)

Analytical Optimum f_{sw} vs Experimental



P_P (kW)	f_{swBest} (kHz)		
	Experimental		Analytical
	Charge	Discharge	Average
0.5	8	8	7.45
1	7	7.5	6.84
1.5	7	6	6.44
2	6	6	6.16

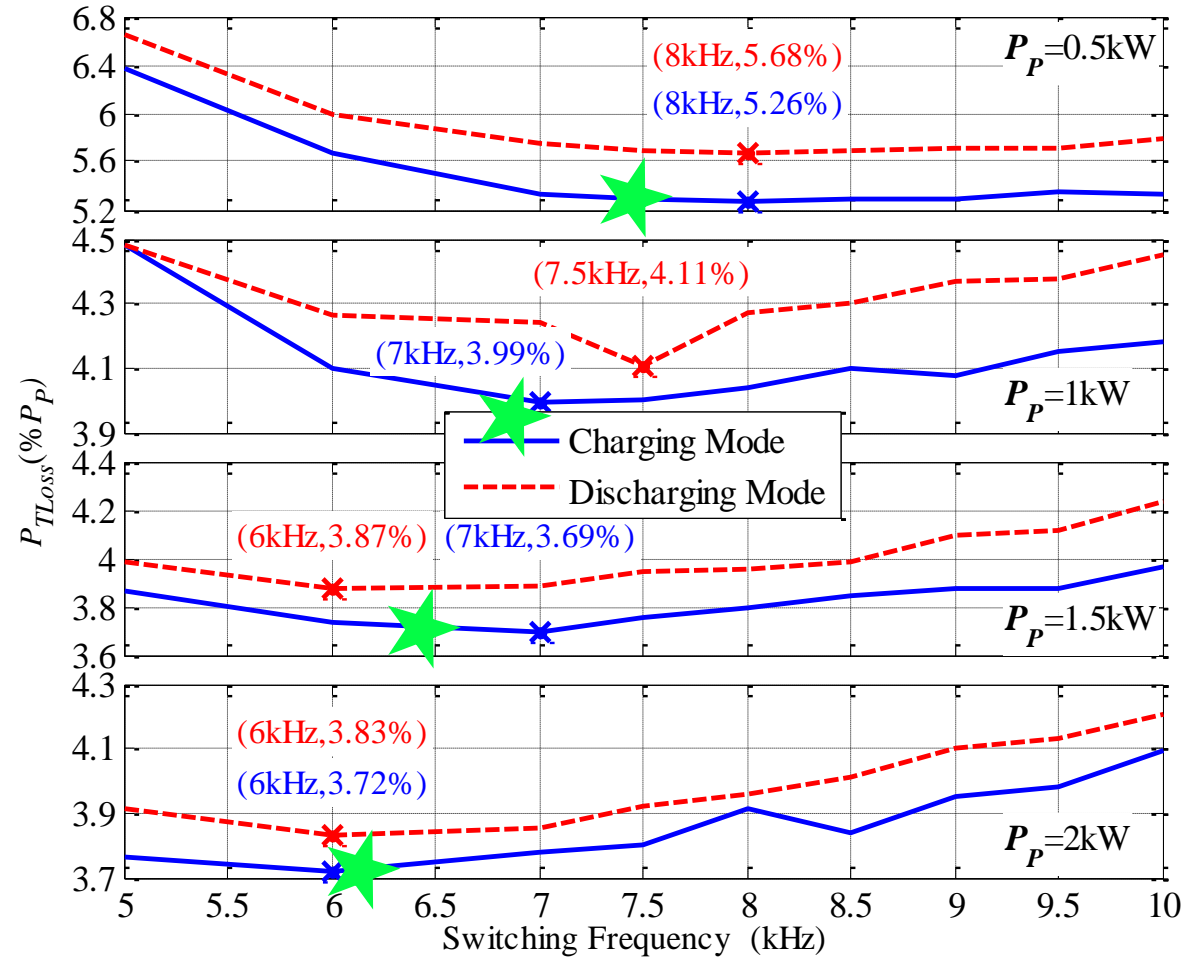The analytical f_{swBest} is very close to the experimental




- The optimum switching frequency reduces as the processing power increases
- Achieve round-trip efficiency of 92.5% at 1.5-2kW (drops to 89% @0.5kW)

Breakdown of Power Loss @ P_N



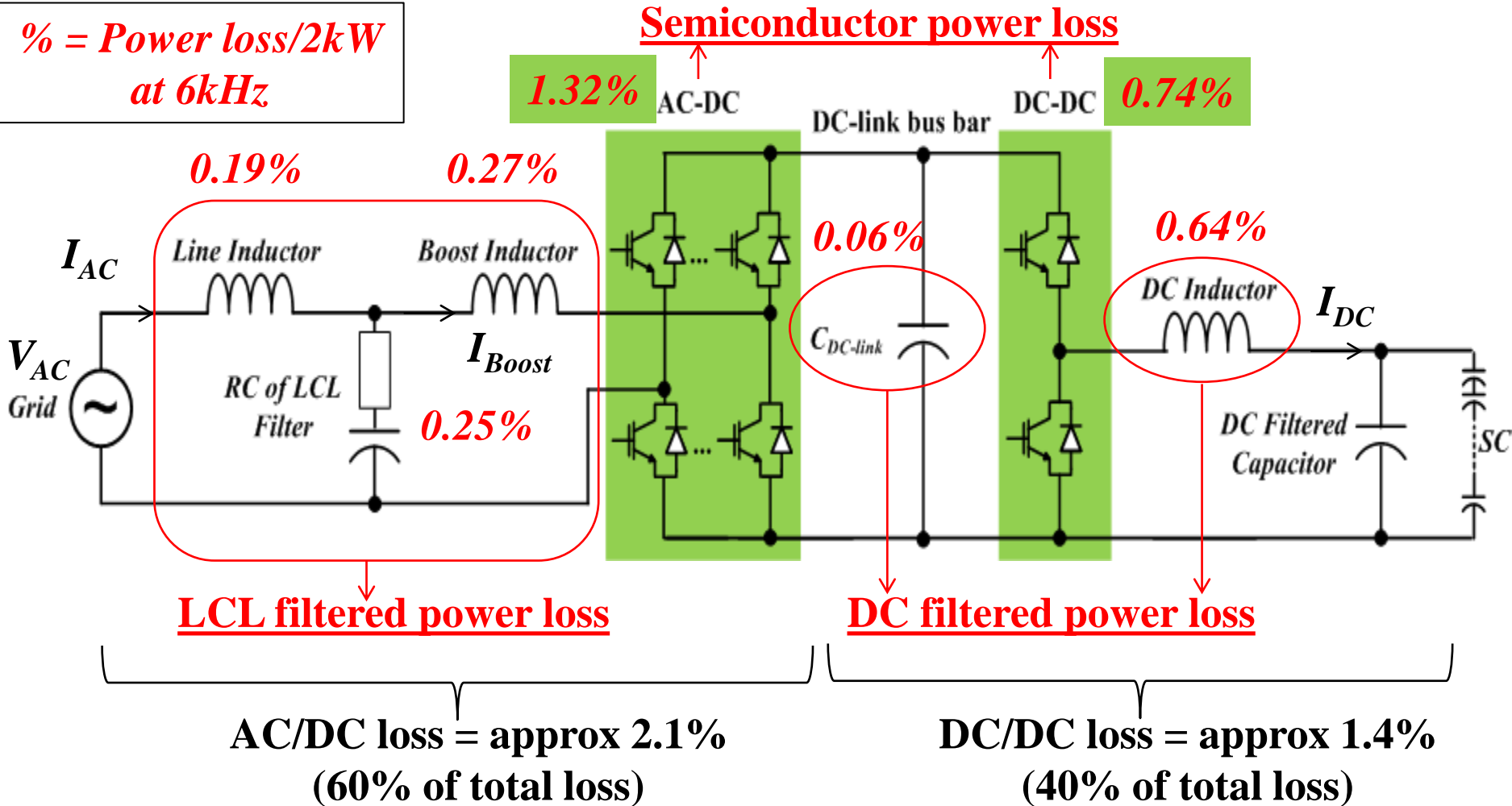$\% = \text{Power loss}/2\text{kW}$
at 6kHz







Further investigation in improving efficiency of each stage is carried out
This includes new topologies and assumes the redesign of passive components⁷

Inverter Improvements: Single Stage vs Two Stage Approach



Potential Benefit: - removes losses associated with the DC/DC stage

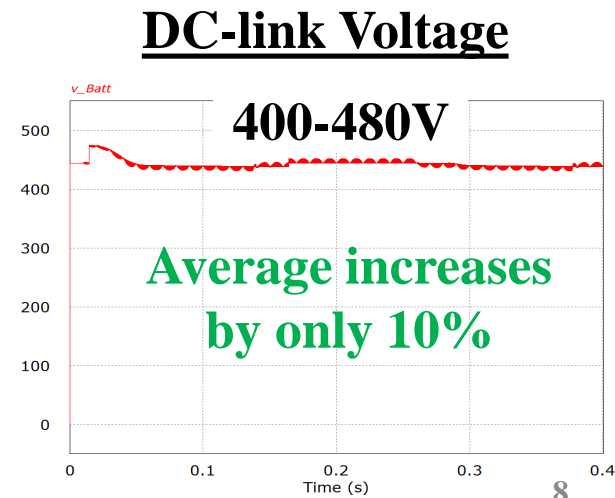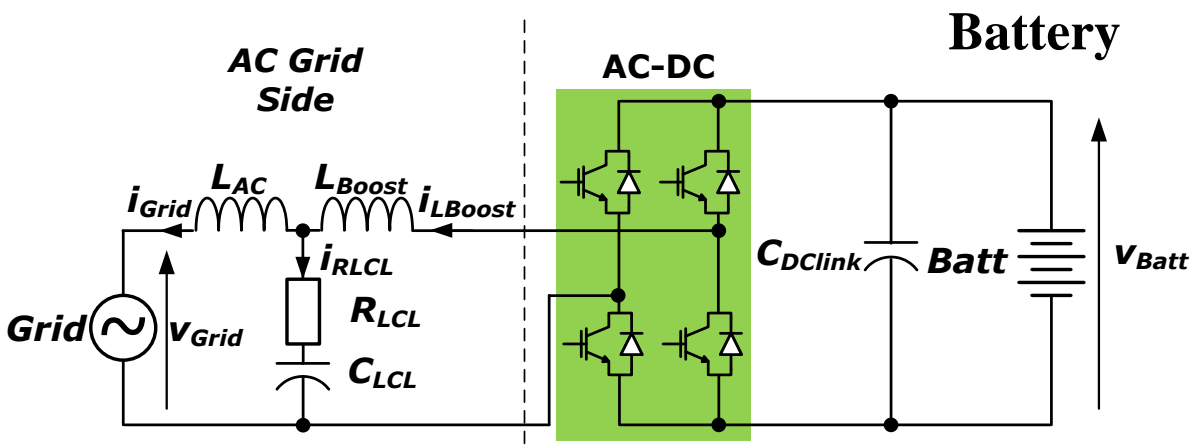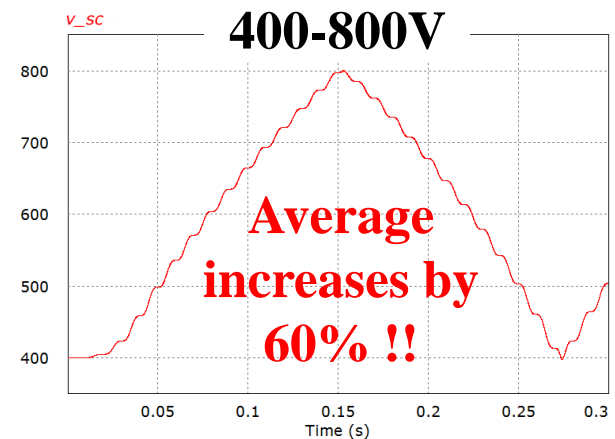
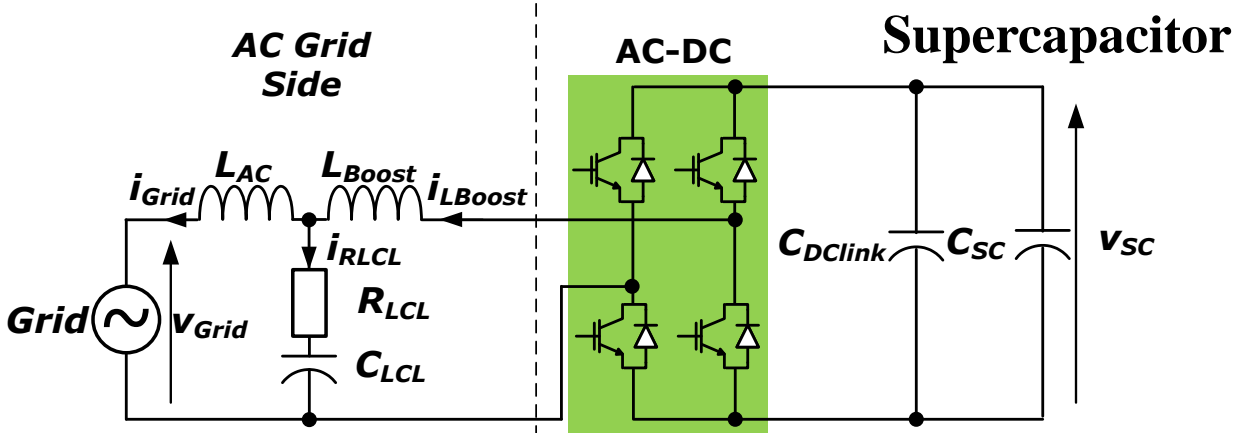
Potential Problem: - switching losses and core/high frequency losses in inductors of AC/DC inverter will increase



Inverter Improvements: Asymmetric Leg & Modulation



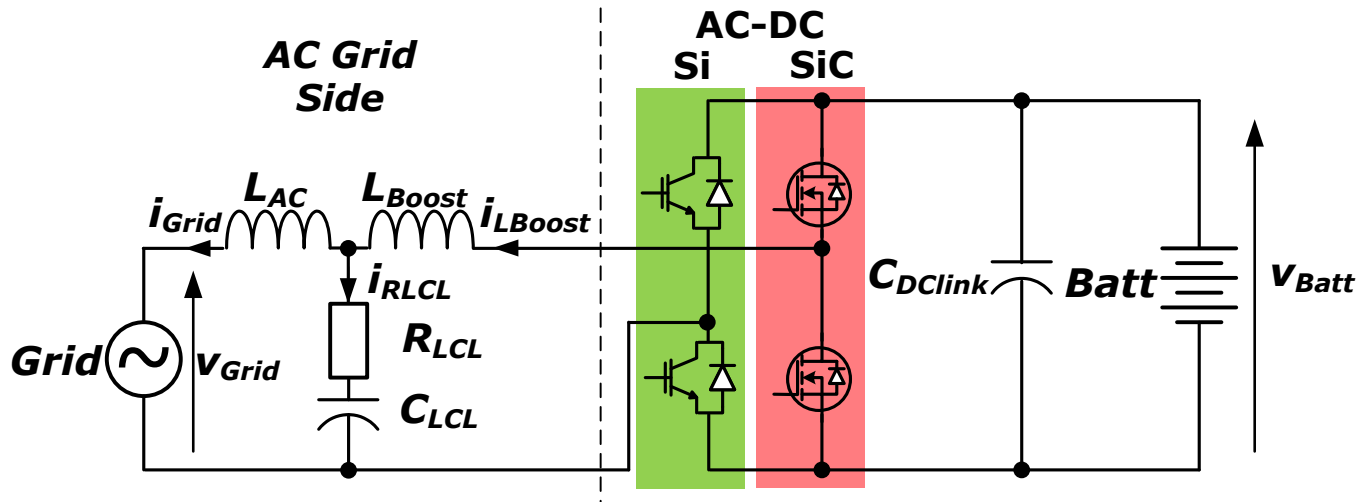 
- Potential Benefit:**
- moves all switching losses in one of the legs
 - then SiC switches can be used in the stressed leg
 - overall could save switching losses with smallest extra cost




Power Loss Comparison of AC/DC Inverter Improvements



25% Power (0.5kW)

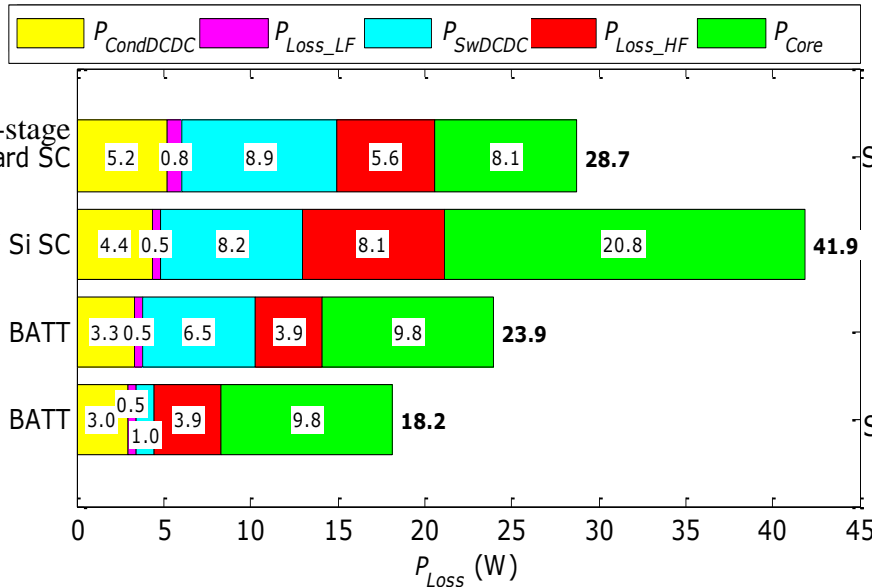

100% Power (2kW)

 





- Single stage + SC in DC-link experiences higher losses due to extra losses in passive components, whilst semiconductor losses in 1-stage/4 switches are in fact smaller than in 2-stage/6 switches
- Use of SiC in one leg (not shown) may further reduce switching losses by 20W making the single stage topology more efficient than 2-stage (70W compared to 73W)
- Use of a storage device with narrow voltage range (battery) may enable cheaper and/or more efficient conversion: silicon (53W) and SiC (46W) compared to 73W
- Advantage of SiC is not so obvious unless f_{sw} needs to be further increased

Improvement in the DC/DC Converter: Use Interleaving



Potential Benefit: - size of L can be reduced w/o increasing f_{sw}

 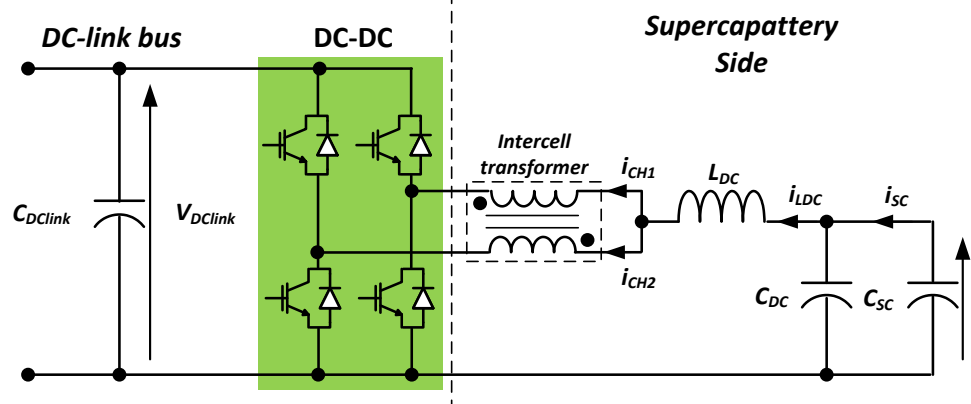 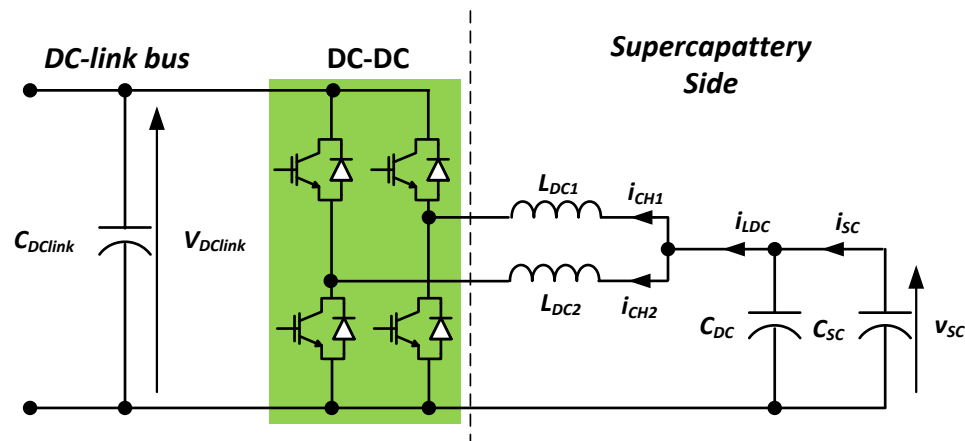
Potential Problem: - current ripple in L will increase (higher HF losses in L)




Improvement in the DC/DC Converter: Use Multilevel DC/DC Converter



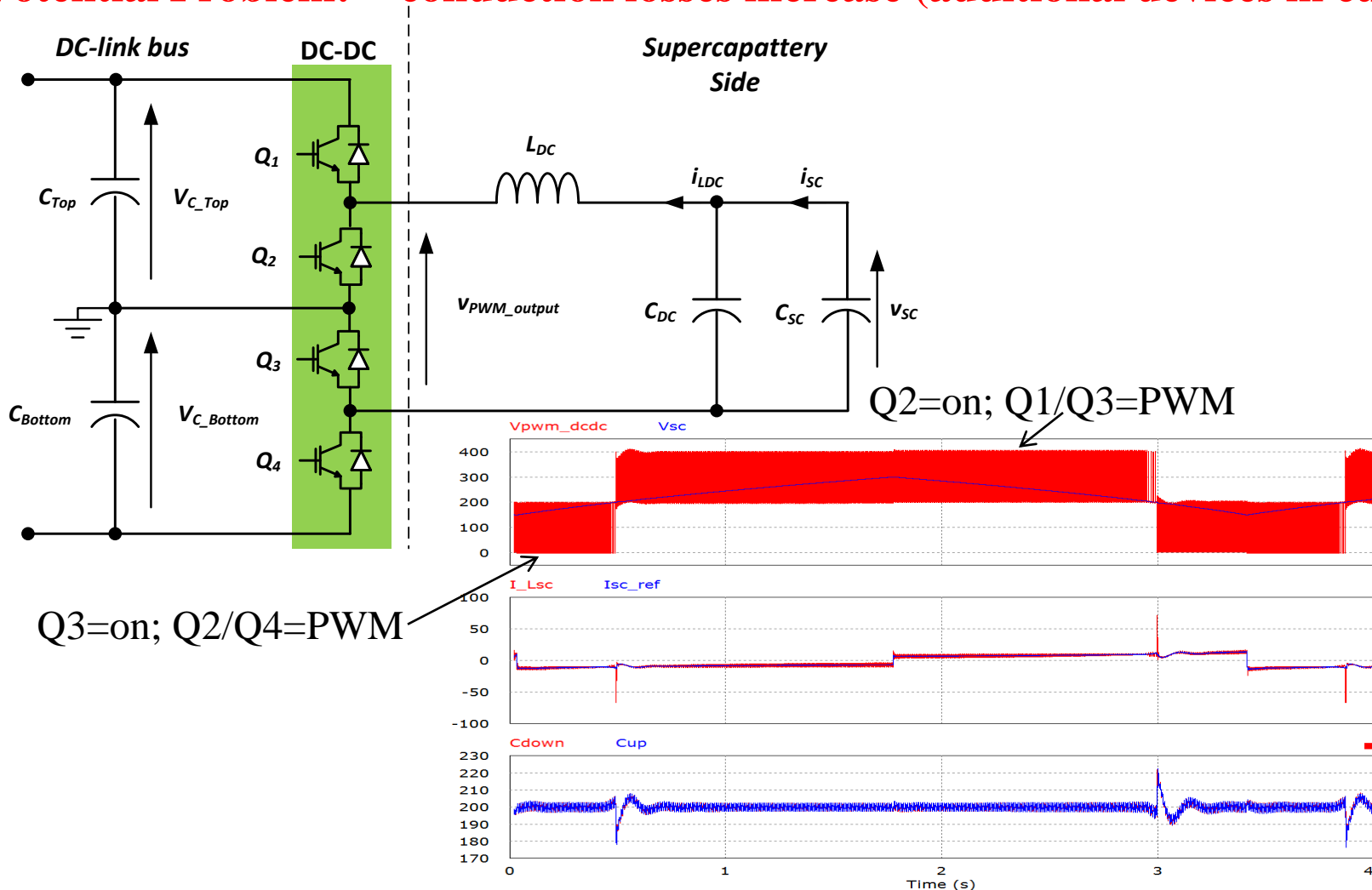- Potential Benefit:** - size of L_{DC} and switching losses can be reduced (switch $\frac{1}{2} V_{dc}$)
- Potential Problem:** - conduction losses increase (additional devices in current path)




DC/DC stage Power Loss Comparison

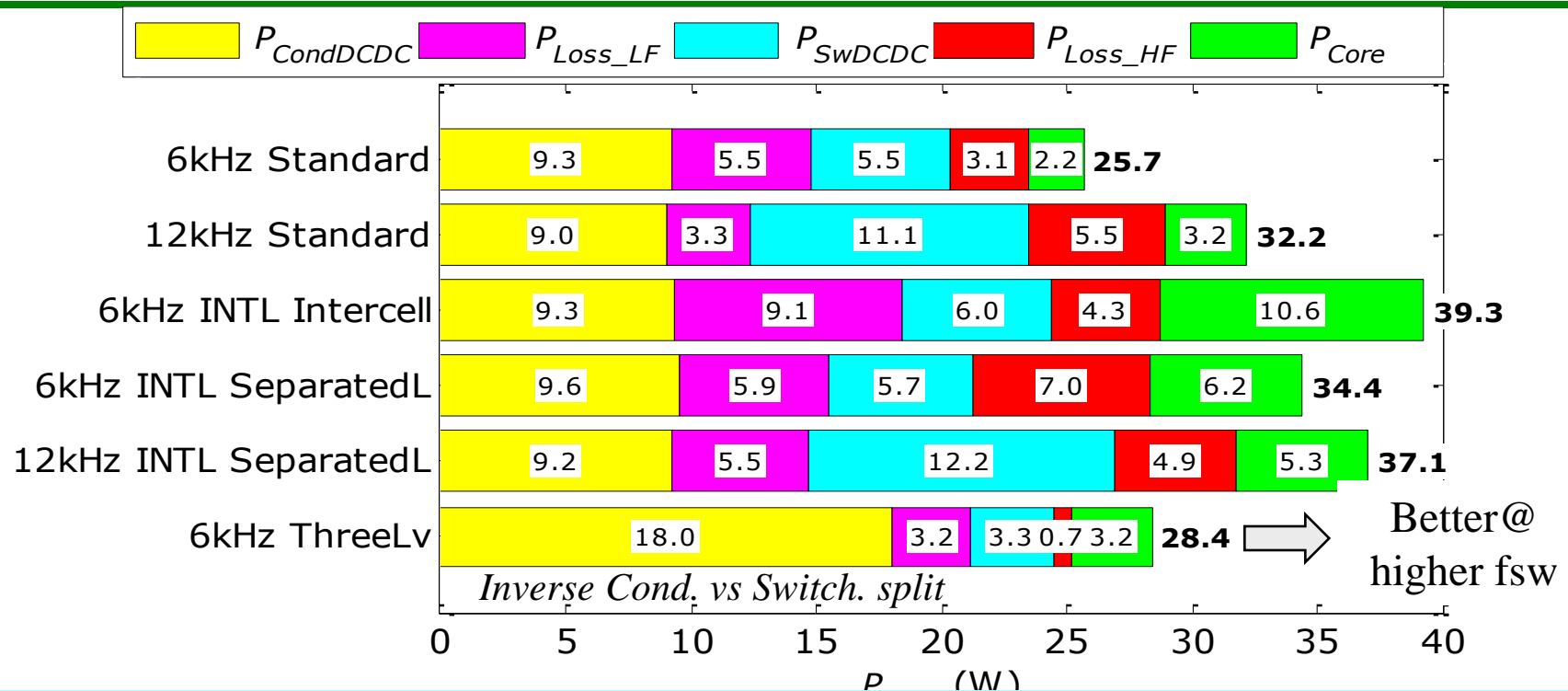

- The standard configuration remains the most efficient but currently has a problem DC/DC causes too much noise
- Increase Standard f_{sw} to 12kHz causes an increase of only 6.5W (0.3%) but still remain the most efficient at 12kHz
- If reduction in physical size is required (of L_{dc}), switching faster and adopting a more complex converter may be more efficient solution as well 3Lv@ $f_{sw}>12kHz$

Use SiC devices in DC/DC converter

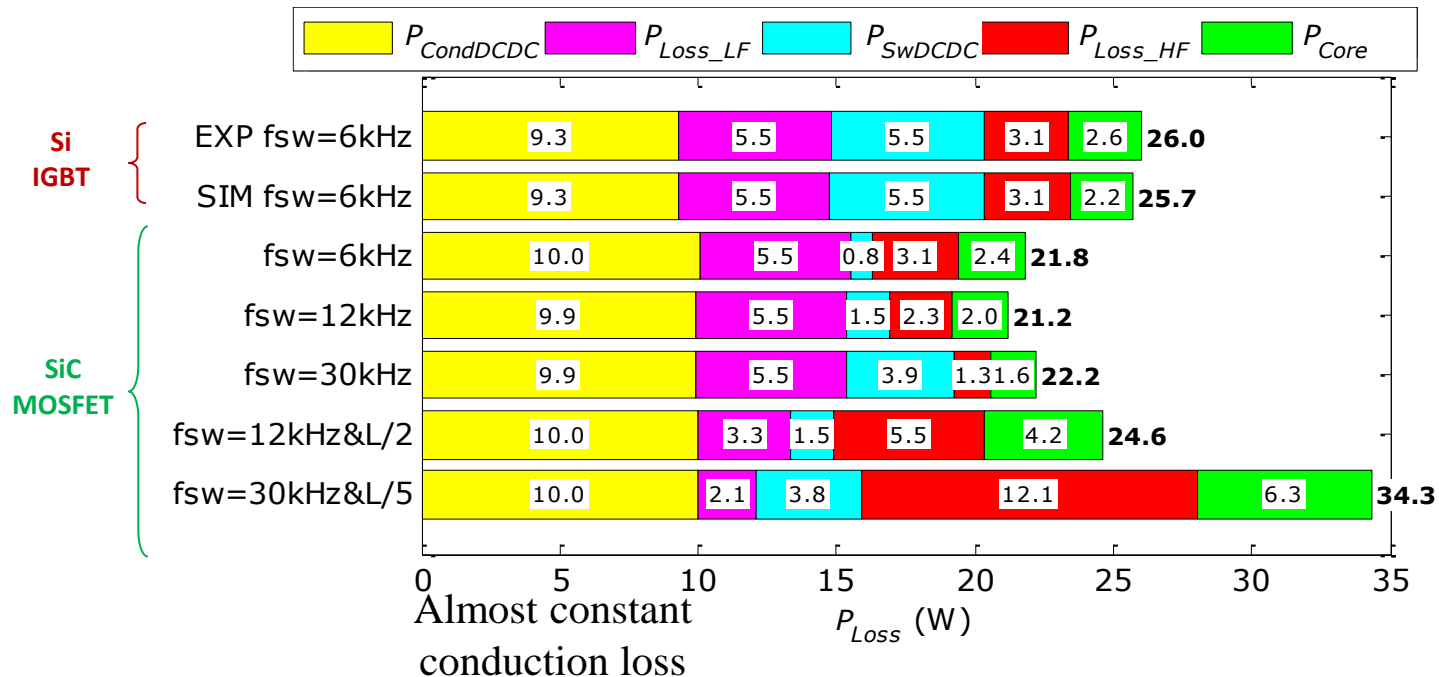

- SiC devices allow for a small decrease (-4W) of losses at low switching frequency; The switching stress will be insignificant and equivalent to oversizing the converter/poor utilisation of devices
- Choosing to sacrifice slightly efficiency (+8W loss) for the sake of increasing significantly the power density (much smaller 0.2L-size) can be an option
- Similar losses/efficiencies are achievable with moderate increase of fsw (12-20kHz) and moderate decrease to 0.4-0.5 of L-size

- State of the art switches and converter technologies can provide reasonable cost & performance ($\eta=92.5\%$ RT) in energy storage apps
- Analytical models of losses can help find the switching frequency optimum at optimise losses at different loading levels
- Further improving the efficiency of the power converters have been investigated including:
 - Employ new SiC semiconductor technology to reduce switching losses and by switching faster, to reduce magnetic component size
 - Employ more complex topology (e.g. multi-level, interleaved, etc) to reduce filter size (smaller voltage ripple or period)
 - Most approaches didn't actually reduced losses but may be the key to reduce physical size of the converter

Acknowledgement - The project this report is based on was funded by E.ON as part of the E.ON International Research Initiative. Responsibility for the content of this publication lies with the author.